

Chapter 5 Summary

Analog Signal Processing Using Operational Amplifiers

gain:

$$A_v = \frac{V_{\text{out}}}{V_{\text{in}}}$$

op amp ideal model:

1. $I_+ = I_- = 0$
2. $V_+ = V_-$
3. V_{out} is independent of I_{out} .
4. negative feedback is required

inverting amplifier:

$$\frac{V_{\text{out}}}{V_{\text{in}}} = -\frac{R_F}{R}$$

noninverting amplifier:

$$\frac{V_{\text{out}}}{V_{\text{in}}} = 1 + \frac{R_F}{R}$$

buffer/follower:

$$V_{\text{out}} = V_{\text{in}}$$

summer with $R_1 = R_2 = R_F$: $V_{\text{out}} = -(V_1 + V_2)$

difference amplifier with $R_1 = R_2 = R$:

$$V_{\text{out}} = \frac{R_F}{R}(V_2 - V_1)$$

instrumentation amplifier:

$$V_{\text{out}} = \left[\frac{R_4}{R_3} \left(1 + 2 \frac{R_2}{R_1} \right) \right] (V_2 - V_1)$$

integrator:

$$V_{\text{out}}(t) = -\frac{1}{RC} \int_0^t V_{\text{in}}(\tau) d\tau$$

differentiator:

$$V_{\text{out}} = -RC \frac{dV_{\text{in}}}{dt}$$

sample and hold:

$$V_{\text{out}}(t - t_{\text{sampled}}) = V_{\text{in}}(t_{\text{sampled}})$$


comparator:

$$V_{\text{out}} = \begin{cases} +V_{\text{sat}} & V_{\text{in}} > V_{\text{ref}} \\ -V_{\text{sat}} & V_{\text{in}} < V_{\text{ref}} \end{cases}$$

real op amp characteristics:

maximum voltage swing: -13.6 V to 13.6 V

frequency response:

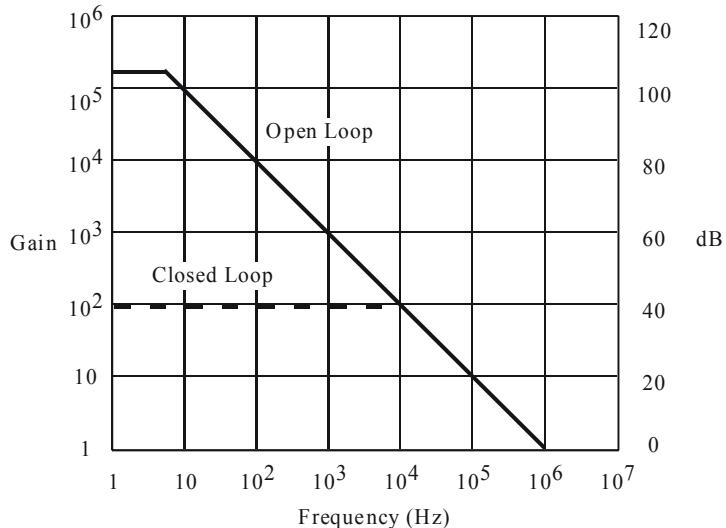

maximum output current: $I_{out} < I_{osc}$